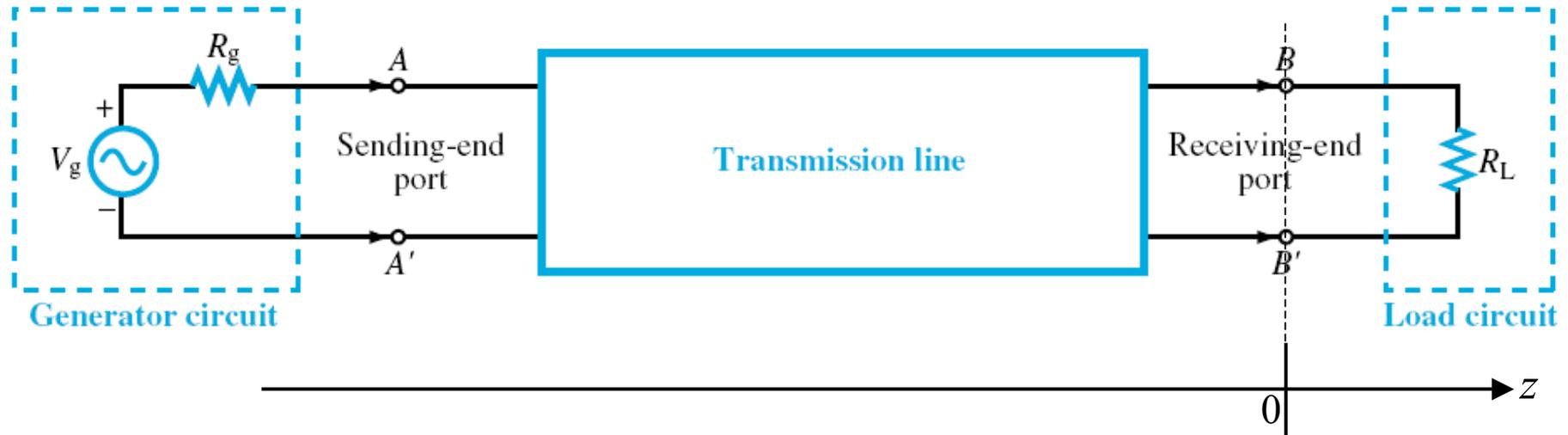


# Transmission Lines – Basic Theories

## 1 Introduction

At high frequencies, the wavelength is much smaller than the circuit size, resulting in different phases at different locations in the circuit.


Quasi-static circuit theory cannot be applied. We need to use transmission line theory.




**A transmission line is a two-port network connecting a generator circuit at the sending end to a load at the receiving end.**

Unlike in circuit theory, the **length** of a transmission line is of utmost importance in transmission line analysis.


## 2 Common Types of Transmission Lines

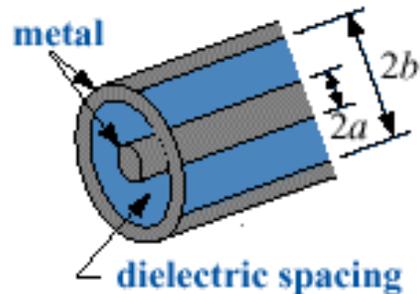


(a) Coaxial line

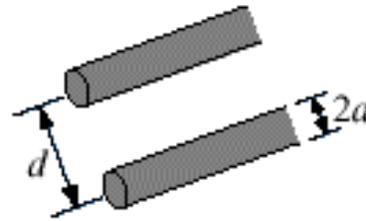


(b) Two-wire line

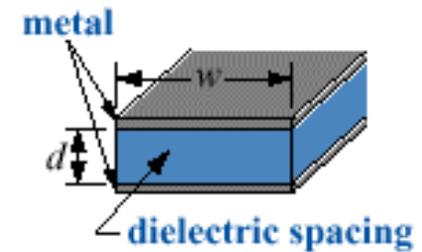

(c) Parallel-plate line

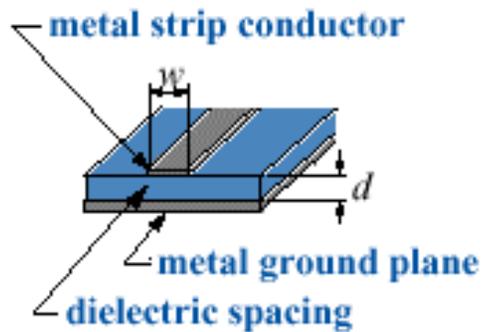

(d) Microstrip line

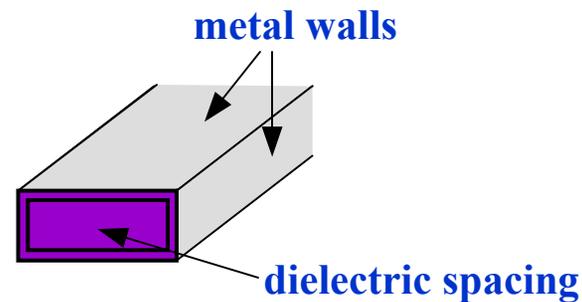


(e) Waveguide

We focus on studying the coaxial and the two-wire transmission lines.

## 3 AC Steady-State Analysis
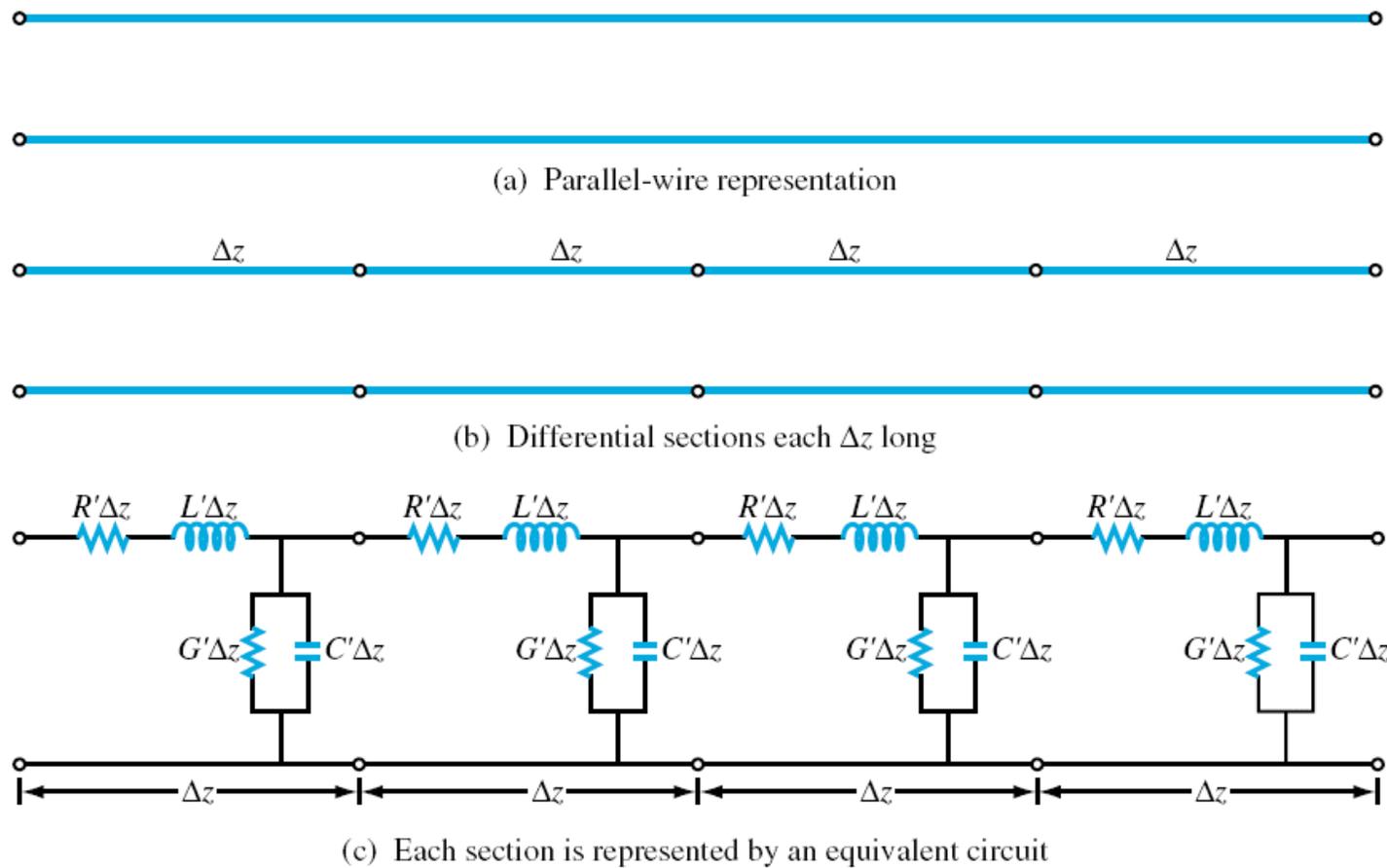
### 3.1 Distributed parameter representation



We use the following distributed parameters to characterize the circuit properties of a transmission line.

$R'$  = resistance per unit length, ( $\Omega/\mathbf{m}$ )

$L'$  = inductance per unit length, ( $\mathbf{H}/\mathbf{m}$ )

$G'$  = conductance per unit length, ( $\mathbf{S}/\mathbf{m}$ )

$C'$  = capacitance per unit length, ( $\mathbf{F}/\mathbf{m}$ )

$\Delta z$  = increment of length, ( $\mathbf{m}$ )

These parameters are related to the physical properties of the material filling the space between the two wires.

$$L' C' = \mu \varepsilon \qquad \frac{G'}{C'} = \frac{\sigma}{\varepsilon}$$

(See Text Book No.3,  
pp. 432-433)

where  $\mu$ ,  $\varepsilon$ ,  $\sigma$  = permittivity, permeability, conductivity of the surrounding medium.


For the coaxial and two-wire transmission lines, the distributed parameters are related to the physical properties and geometrical dimensions as follows:

Parameter	Coaxial	Two Wire
$R'$	$\frac{R_s}{2\pi} \left( \frac{1}{a} + \frac{1}{b} \right)$	$\frac{R_s}{\pi a}$
$L'$	$\frac{\mu}{2\pi} \ln(b/a)$	$\frac{\mu}{\pi} \ln \left[ (d/2a) + \sqrt{(d/2a)^2 - 1} \right]$
$G'$	$\frac{2\pi\sigma}{\ln(b/a)}$	$\frac{\pi\sigma}{\ln \left[ (d/2a) + \sqrt{(d/2a)^2 - 1} \right]}$
$C'$	$\frac{2\pi\epsilon}{\ln(b/a)}$	$\frac{\pi\epsilon}{\ln \left[ (d/2a) + \sqrt{(d/2a)^2 - 1} \right]}$

Surface resistivity of the conductors (See Text Book No.3, pp. 445-447)
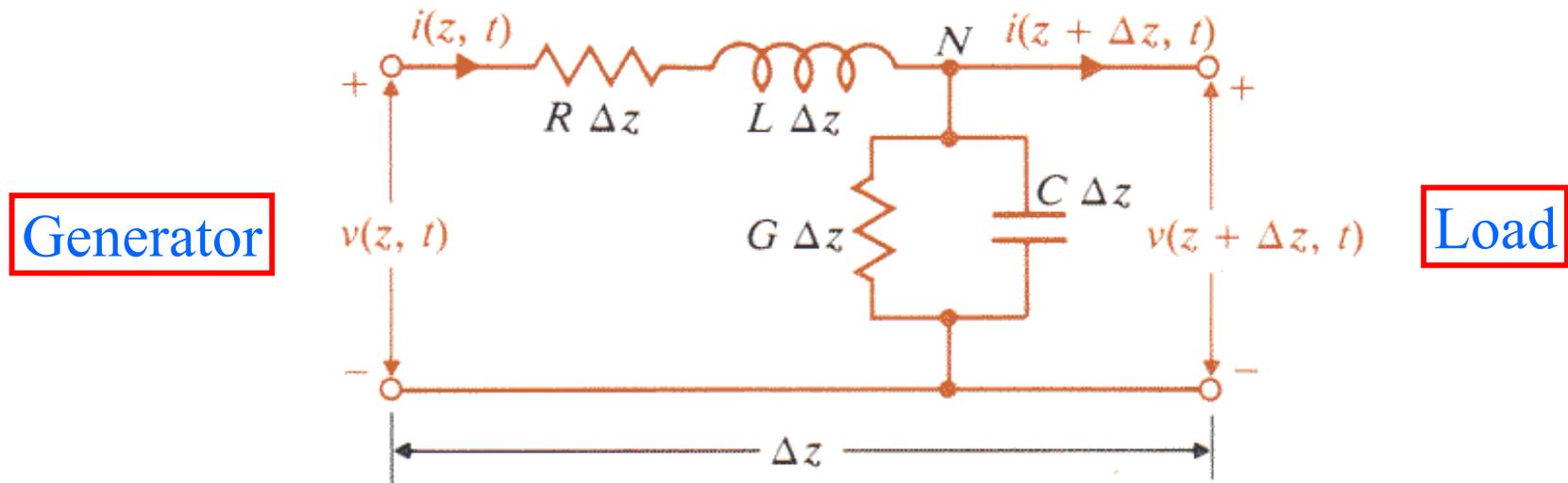
## 3.2 Equations and solutions

Consider a short section  $\Delta z$  of a transmission line (dropping the primes on  $R'$ ,  $L'$ ,  $G'$ ,  $C'$  hereafter) :



Using **KVL** and **KCL** circuit theorems, we can derive the following differential equations for this section of transmission line.

$$v(z, t) - R\Delta z i(z, t) - L\Delta z \frac{\partial i(z, t)}{\partial t} - v(z + \Delta z, t) = 0$$

$$i(z, t) - G\Delta z v(z + \Delta z, t) - C\Delta z \frac{\partial v(z + \Delta z, t)}{\partial t} - i(z + \Delta z, t) = 0$$

By letting  $\Delta z \rightarrow 0$ , these lead to coupled equations:

$$-\frac{\partial v(z, t)}{\partial z} = Ri(z, t) + L \frac{\partial i(z, t)}{\partial t}$$

$$-\frac{\partial i(z, t)}{\partial z} = Gv(z, t) + C \frac{\partial v(z, t)}{\partial t}$$

**General Transmission Line Equations – Coupled!**

For sinusoidal varying voltages and currents, we can use phasor forms.

$$v(z, t) = \text{Re}\{V(z)e^{j\omega t}\}$$

$$i(z, t) = \text{Re}\{I(z)e^{j\omega t}\}$$

$V(z)$  and  $I(z)$  are called **phasors** of  $v(z, t)$  and  $i(z, t)$ . In terms of phasors, the coupled equations can be written as:

$$-\frac{dV(z)}{dz} = (R + j\omega L)I(z)$$

$$-\frac{dI(z)}{dz} = (G + j\omega C)V(z)$$

After decoupling,

$$\frac{d^2 V(z)}{dz^2} = \gamma^2 V(z)$$

$$\frac{d^2 I(z)}{dz^2} = \gamma^2 I(z)$$

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$\gamma$  is the complex propagation constant whose real part  $\alpha$  is the **attenuation constant** (Np/m) and whose imaginary part  $\beta$  is the **phase constant** (rad/m). Generally, these quantities are functions of  $\omega$ .

## Solutions to transmission line equations:

Forward travelling wave.  $\rightarrow$

$$V(z) = V^+(z) + V^-(z)$$
$$= V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}$$

$\leftarrow$  Backward travelling wave.

$$I(z) = I^+(z) + I^-(z)$$
$$= I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z}$$

$V_0^+, V_0^-, I_0^+, I_0^-$  = wave amplitudes in the forward and backward directions at  $z = 0$ . (They are complex numbers in general.)

## 4 Transmission Line Parameters

From the solutions to the transmission line equations, it can be shown (using the coupled transmission line equations) that:

$$\frac{V_0^+}{I_0^+} = -\frac{V_0^-}{I_0^-} = \frac{R + j\omega L}{\gamma}$$

This ratio is called characteristic impedance  $Z_0$ .

$$Z_0 = \frac{R + j\omega L}{\gamma} = \frac{\gamma}{G + j\omega C} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$Z_0$  and  $\gamma$  are the two most important parameters of a transmission line. They depend on the distributed parameters ( $RLGC$ ) of the line itself and  $\omega$  but not the length of the line.

## Parameters for lossless transmission lines

For lossless transmission lines,  $R = G = 0$ .

$$\alpha = 0$$

$$\beta = \omega\sqrt{LC} = \omega\sqrt{\mu\varepsilon}$$

$$u_p = \text{phase velocity} = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\mu\varepsilon}}$$

$\gamma$  = complex propagation constant

$$= j\beta = j\omega\sqrt{\mu\varepsilon} = j2\pi f\sqrt{\mu\varepsilon} = j\frac{2\pi}{\lambda} = jk$$

$\lambda$  = wavelength along the transmission line

$$= \frac{u_p}{f} = \frac{1}{f\sqrt{\mu\varepsilon}} = \frac{\omega}{f\beta} = \frac{2\pi}{\beta} = \frac{1}{f\sqrt{LC}}$$

$Z_0$  = characteristic impedance

$$= \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$
$$= \sqrt{\frac{L}{C}}$$

Voltage and current along the line:

$$V(z) = V_0^+ e^{-jkz} + V_0^- e^{jkz}$$

$$I(z) = I_0^+ e^{-jkz} + I_0^- e^{jkz}$$

Define a reflection coefficient at  $z = 0$  as  $\Gamma_L$ :

$$\begin{aligned} \Gamma_L &= \frac{\text{reflected voltage at } z = 0}{\text{incident voltage at } z = 0} \\ &= \frac{V_0^- e^{jk \times 0}}{V_0^+ e^{-jk \times 0}} = \frac{V_0^-}{V_0^+} = |\Gamma_L| e^{j\theta_L} \end{aligned}$$

In terms of the reflection coefficient  $\Gamma_L$ , the total voltage and current can be written as:

$$\begin{aligned}
 V(z) &= V_0^+ e^{-jkz} + V_0^- e^{jkz} \\
 &= V_0^+ e^{-jkz} \left( 1 + \frac{V_0^-}{V_0^+} e^{2jkz} \right) \\
 &= V_0^+ e^{-jkz} \left( 1 + \Gamma_L e^{2jkz} \right)
 \end{aligned}
 \qquad
 \begin{aligned}
 I(z) &= \frac{V_0^+}{Z_0} e^{-jkz} - \frac{V_0^-}{Z_0} e^{jkz} \\
 &= \frac{V_0^+}{Z_0} e^{-jkz} \left( 1 - \frac{V_0^-}{V_0^+} e^{2jkz} \right) \\
 &= I_0^+ e^{-jkz} \left( 1 - \Gamma_L e^{2jkz} \right)
 \end{aligned}$$

In subsequent analyses, we will consider only lossless transmission lines.

## 5 Infinitely Long Transmission Line

For an infinitely long transmission line, there can be no reflected wave (backward travelling wave). So for an infinite long transmission line, there is only a forward travelling wave.


$$V(z) = V^+(z) = V_0^+ e^{-jkz}$$

$$I(z) = I^+(z) = I_0^+ e^{-jkz}$$

$$Z(z) = \frac{V(z)}{I(z)} = \frac{V_0^+(z)}{I_0^+(z)} = Z_0$$

$$\Gamma_L = 0$$

## 6 Terminated Transmission Line

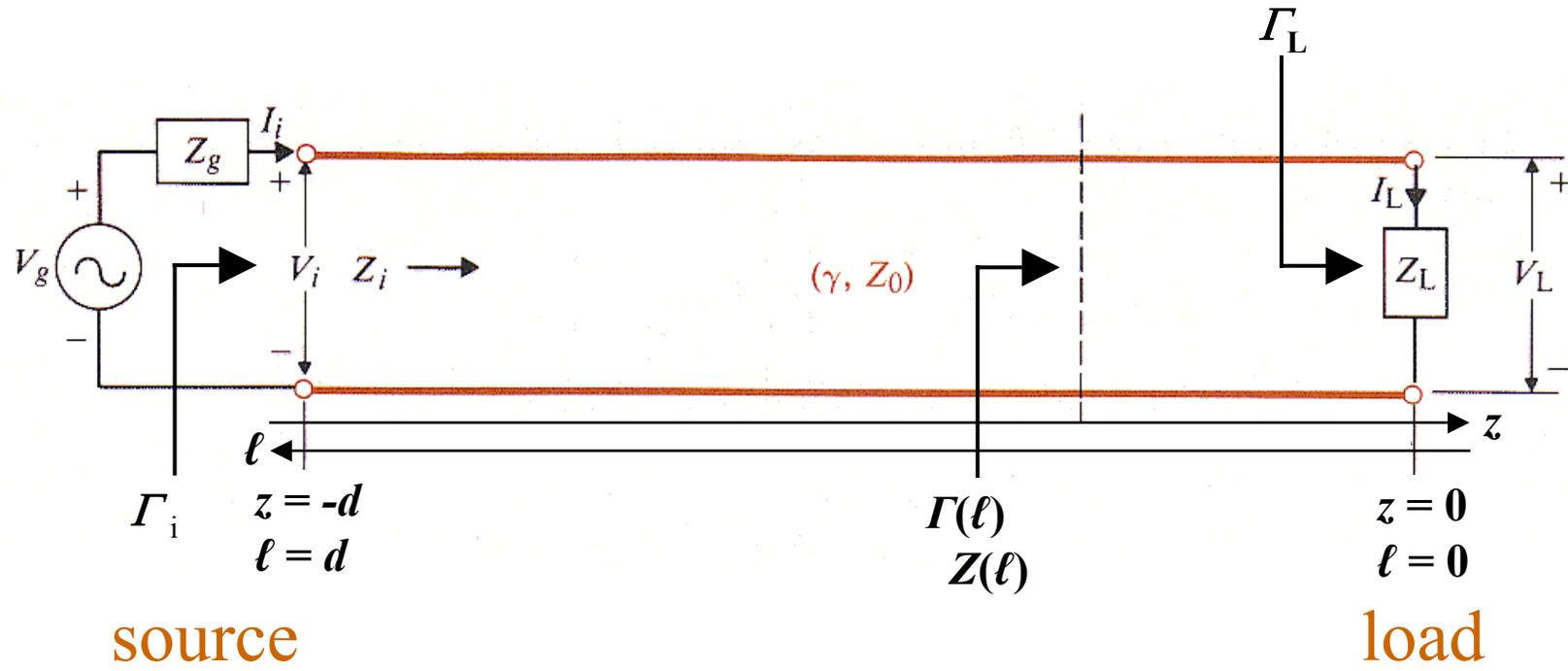

Note the two coordinate systems and their relation:

$z$  = measuring from the left to the right

$\ell$  = measuring from the right to the left

$$\ell = -z$$

In the  $z$  coordinate system,

$$V_0^+ e^{-jkz} + V_0^- e^{jkz} = V(z)$$

$$I_0^+ e^{-jkz} + I_0^- e^{jkz} = I(z)$$

In the  $\ell$  ( $\ell = -z$ ) coordinate system,

$$V_0^+ e^{jkl} + V_0^- e^{-jkl} = V(\ell)$$

$$I_0^+ e^{jkl} + I_0^- e^{-jkl} = I(\ell)$$

We will use the  $\ell$  coordinate system in subsequent analyses.

The characteristic impedance in the  $\ell$  coordinate system is:

$$\frac{V_0^+}{I_0^+} = Z_0$$

The reflection coefficient at  $\ell = 0$  in the  $\ell$  coordinate system is:

$$\Gamma(\ell = 0) = \frac{V_0^- e^{-jk \times 0}}{V_0^+ e^{jk \times 0}} = \Gamma_L$$

As  $\Gamma_L$  is obtained at  $\ell = 0$  (the load position), it is called the reflection coefficient at the load.

At the position of the load ( $\ell = 0$ ), the voltage is  $V_L$  and the current is  $I_L$ . Then we have:

$$V_0^+ + V_0^- = V_L$$

$$\frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0} = I_L$$

$$\frac{V_L}{I_L} = Z_L$$

Solve these two equations, we have:

$$V_0^+ = \frac{1}{2} I_L (Z_L + Z_0)$$

$$V_0^- = \frac{1}{2} I_L (Z_L - Z_0)$$

Putting the expressions for  $V_0^+$  and  $V_0^-$  into the equations for the voltage and current, we have:

$$\begin{aligned} V(\ell) &= \frac{1}{2} I_L \left[ Z_L (e^{jkl} + e^{-jkl}) + Z_0 (e^{jkl} - e^{-jkl}) \right] \\ &= I_L [Z_L \cos(k\ell) + jZ_0 \sin(k\ell)] \end{aligned}$$

$$\begin{aligned} I(\ell) &= \frac{1}{2} \frac{I_L}{Z_0} \left[ Z_L (e^{jkl} - e^{-jkl}) + Z_0 (e^{jkl} + e^{-jkl}) \right] \\ &= \frac{I_L}{Z_0} [Z_0 \cos(k\ell) + jZ_L \sin(k\ell)] \end{aligned}$$

Using  $V(\ell)$  and  $I(\ell)$ , we can obtain the impedance  $Z(\ell)$  at an arbitrary point  $\ell$  on the transmission line as:

$$Z(\ell) = \frac{V(\ell)}{I(\ell)} = Z_0 \frac{Z_L + jZ_0 \tan(k\ell)}{Z_0 + jZ_L \tan(k\ell)}$$

The reflection coefficient at the load  $\Gamma_L$  can be expressed as:

$$\Gamma_L = \frac{V_0^-}{V_0^+} = \frac{\frac{1}{2} I_L (Z_L - Z_0)}{\frac{1}{2} I_L (Z_L + Z_0)} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

In fact, we can further define a reflection coefficient  $\Gamma(\ell)$  at any point  $\ell$  on the transmission line by:

$$\begin{aligned}\Gamma(\ell) &= \frac{\text{reflected voltage at point } \ell}{\text{incident voltage at point } \ell} \\ &= \frac{V_0^- e^{-jkl}}{V_0^+ e^{jkl}} = \frac{V_0^-}{V_0^+} e^{-j2kl} = \Gamma_L e^{-j2kl}\end{aligned}$$

As we know (by solving the two equations on page 22 with  $\ell \neq 0$ ):

$$V_0^+ e^{jkl} = \frac{1}{2} I(\ell)(Z(\ell) + Z_0)$$

$$V_0^- e^{-jkl} = \frac{1}{2} I(\ell)(Z(\ell) - Z_0)$$

Therefore, alternatively we can write,

$$\Gamma(\ell) = \frac{\frac{1}{2} I(\ell)[Z(\ell) - Z_0]}{\frac{1}{2} I(\ell)[Z(\ell) + Z_0]} = \frac{Z(\ell) - Z_0}{Z(\ell) + Z_0}$$


Then,

$$Z(\ell) = Z_0 \frac{1 + \Gamma(\ell)}{1 - \Gamma(\ell)}$$

At the position of the generator ( $\ell = d$ ),

$$Z_i = Z(\ell = d) = Z_0 \frac{Z_L + jZ_0 \tan(kd)}{Z_0 + jZ_L \tan(kd)}$$

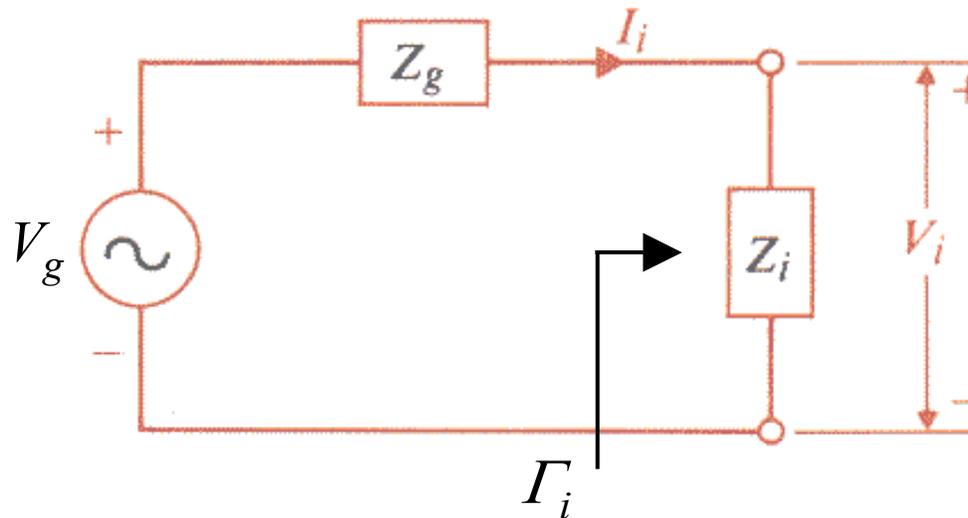
$$\Gamma(\ell = d) = \Gamma_i = \frac{Z_i - Z_0}{Z_i + Z_0} = \Gamma_L e^{-j2kd}$$



## Example 1

A  $100\text{-}\Omega$  transmission line is connected to a load consisted of a  $50\text{-}\Omega$  resistor in series with a  $10\text{-pF}$  capacitor.

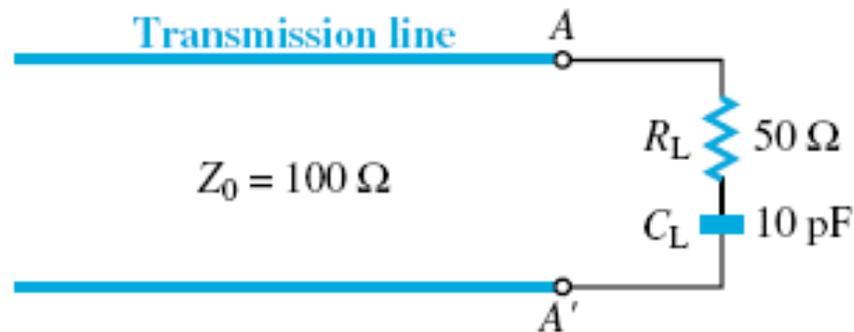- (a) Find the reflection coefficient  $\Gamma_L$  at the load for a  $100\text{-MHz}$  signal.
- (b) Find the impedance  $Z_{in}$  at the input end of the transmission line if its length is  $0.125\lambda$ .



## Solutions

The following information is given

$$R_L = 50\Omega, \quad C_L = 10^{-11}\text{F}, \quad Z_0 = 100\Omega, \quad f = 100\text{MHz} = 10^8\text{Hz}$$

The load impedance is

$$\begin{aligned} Z_L &= R_L - j/\omega C_L \\ &= 50 - j \frac{1}{2\pi \times 10^8 \times 10^{-11}} = 50 - j159 \quad (\Omega) \end{aligned}$$

(a) Voltage reflection coefficient is

$$\Gamma_L = \frac{Z_L / Z_0 - 1}{Z_L / Z_0 + 1} = \frac{0.5 - j1.59 - 1}{0.5 - j1.59 + 1} = 0.76 \angle -60.70^\circ$$

(b)  $d = 0.125 \lambda$

$$\begin{aligned}
 Z_{in} &= Z(\ell = 0.125\lambda) \\
 &= Z_0 \frac{Z_L + jZ_0 \tan(\pi/4)}{Z_0 + jZ_L \tan(\pi/4)} \\
 &= Z_0 \frac{Z_L + jZ_0}{Z_0 + jZ_L} \\
 &= 14.3717 - j25.5544 \quad (\Omega) \\
 &= 29.32 \angle -60.65^\circ \quad (\Omega)
 \end{aligned}$$

Normalized  $z_{in} = 0.1437 - j 0.2555 \Omega$

See animation "Transmission Line Impedance Calculation"

## 6.1 Voltage/current maxima and minima

$$V(\ell) = V_0^+ e^{jkl} + V_0^- e^{-jkl}$$

$$= V_0^+ e^{jkl} \left( 1 + \frac{V_0^-}{V_0^+} e^{-j2kl} \right)$$

$$= V_0^+ e^{jkl} \left( 1 + \Gamma_L e^{-j2kl} \right)$$

$$\Gamma_L = |\Gamma_L| e^{j\theta_L}$$

$$|\Gamma_L| \leq 1$$


$$|V(\ell)| = |V_0^+| \left| 1 + \Gamma_L e^{-j2kl} \right|$$

$$= |V_0^+| \left| 1 + |\Gamma_L| e^{j(\theta_L - 2kl)} \right|$$

$$\Gamma = |\Gamma_L| e^{j(\theta_L - 2kl)}$$

= a complex number

$$= |V_0^+| \left| 1 + \Gamma \right|$$

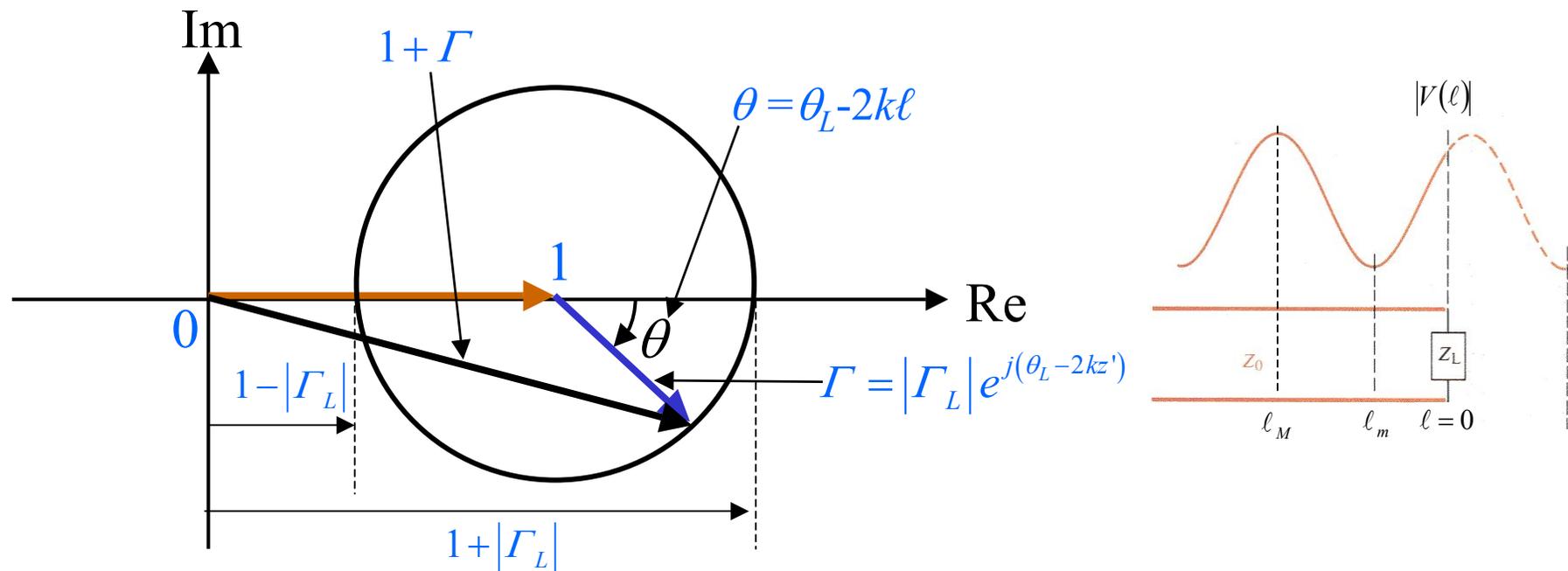

## Complex plane of $(1 + \Gamma)$

See animation “Transmission Line Voltage Maxima and Minima”

$|V(\ell)|$  is maximum when  $|1 + \Gamma| = (1 + |\Gamma_L|)$

$$|V(\ell)|_{\max} \Rightarrow \theta = \theta_L - 2k\ell = -2n\pi$$

$$\Rightarrow \ell_M = \frac{\theta_L \lambda}{4\pi} + \frac{n\lambda}{2}, \quad n = 0, 1, 2, \dots$$

Note:  $\theta_L$  has to be specified in the range  $[-\pi, \pi)$ .

$|V(\ell)|$  is minimum when  $|1 - \Gamma| = (1 - |\Gamma_L|)$

$$|V(\ell)|_{\min} \Rightarrow \theta = \theta_L - 2k\ell = -(2n + 1)\pi$$

$$\Rightarrow \ell_m = \frac{\theta_L \lambda}{4\pi} + \frac{(2n + 1)\lambda}{4}, \quad n = 0, 1, 2, \dots$$

Note:  $\theta_L$  has to be specified in the range  $[-\pi, \pi)$ .

As current is

$$|I(\ell)| = |I_0^+| |1 - \Gamma_L e^{-j2k\ell}|$$

$$= \left| \frac{V_0^+}{Z_0} \right| |1 - \Gamma|$$

Current is maximum when voltage is minimum and minimum when voltage is maximum.

$$|I(\ell)|_{\max} \text{ at } \ell_M = \frac{\theta_L \lambda}{4\pi} + \frac{(2n+1)\lambda}{4}, \quad n = 0, 1, 2, \dots, \text{ with } |\theta_L| \leq \pi$$



$$|I(\ell)|_{\min} \text{ at } \ell_m = \frac{\theta_L \lambda}{4\pi} + \frac{n\lambda}{2}, \quad n = 0, 1, 2, \dots, \text{ with } |\theta_L| \leq \pi$$

Define a voltage standing wave ratio (VSWR) as:

$S =$  voltage standing wave ratio (VSWR)

$$= \frac{|V(\ell)|_{\max}}{|V(\ell)|_{\min}} = \frac{|V_0^+|(1+|\Gamma_L|)}{|V_0^+|(1-|\Gamma_L|)} = \frac{1+|\Gamma_L|}{1-|\Gamma_L|} \quad (\text{dimensionless})$$

$$|\Gamma_L| = \frac{S-1}{S+1}$$

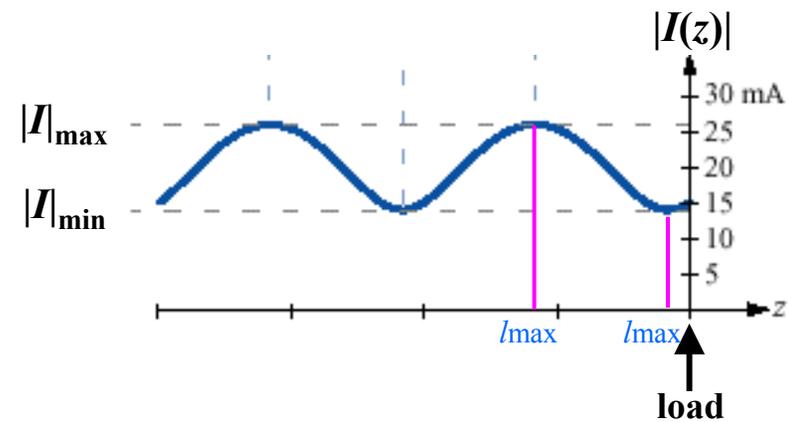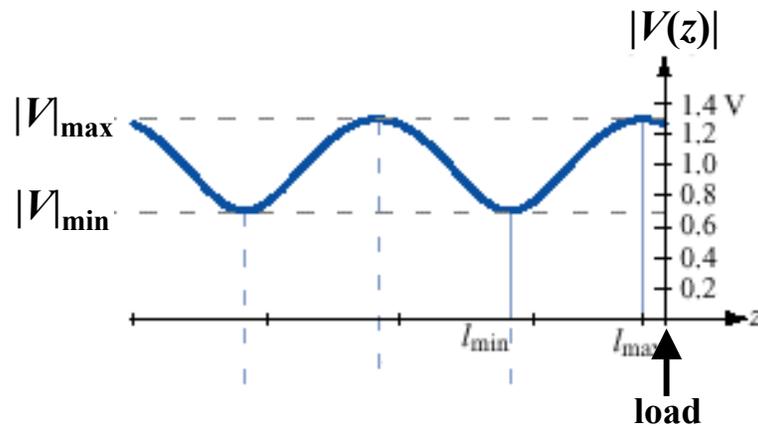

## Special terminations

$\Gamma_L$	$S$	$Z_L$
0	1	$Z_L = Z_0$ (matched)
-1	$\infty$	$Z_L = 0$ (short-circuited)
1	$\infty$	$Z_L = \infty$ (open-circuited)

## 6.2 Power flow in a transmission line

Power flow at any point  $z$  on a transmission line is given by:

$$P_{av}(z) = \frac{1}{2} \operatorname{Re}\{V(z)I^*(z)\}$$

Power delivered by the source:

$$P_s = \frac{1}{2} \operatorname{Re}\{V_g I_i^*\}$$

Power dissipated in the source impedance  $Z_g$ :

$$P_{Z_g} = \frac{1}{2} \operatorname{Re}\{V_{Z_g} I_{Z_g}^*\} = \frac{1}{2} \operatorname{Re}\{Z_g I_i I_i^*\} = \frac{1}{2} |I_i|^2 \operatorname{Re}\{Z_g\}$$

Power input to the transmission line:

$$\begin{aligned}
 P_i &= P_{av}(-d) = \frac{1}{2} \operatorname{Re}\{V(-d)I^*(-d)\} \\
 &= \frac{1}{2} \operatorname{Re}\{V_i I_i^*\} = \frac{1}{2} \operatorname{Re}\{Z_i I_i I_i^*\} = \frac{1}{2} |I_i|^2 \operatorname{Re}\{Z_i\} \\
 &= \frac{1}{2} \operatorname{Re}\left\{V_i \frac{V_i^*}{Z_i^*}\right\} = \frac{1}{2} |V_i|^2 \operatorname{Re}\left\{\frac{1}{Z_i^*}\right\}
 \end{aligned}$$

Power dissipated in the terminal impedance:

$$\begin{aligned}
 P_L &= P_{av}(0) = \frac{1}{2} \operatorname{Re}\{V(0)I^*(0)\} \\
 &= \frac{1}{2} \operatorname{Re}\{V_L I_L^*\} = \frac{1}{2} \operatorname{Re}\{Z_L I_L I_L^*\} = \frac{1}{2} |I_L|^2 \operatorname{Re}\{Z_L\} \\
 &= \frac{1}{2} \operatorname{Re}\left\{V_L \frac{V_L^*}{Z_L^*}\right\} = \frac{1}{2} |V_L|^2 \operatorname{Re}\left\{\frac{1}{Z_L^*}\right\}
 \end{aligned}$$


By the principle of conservation of power:

$$P_s = P_{Z_g} + P_i$$

$$P_i = P_L$$
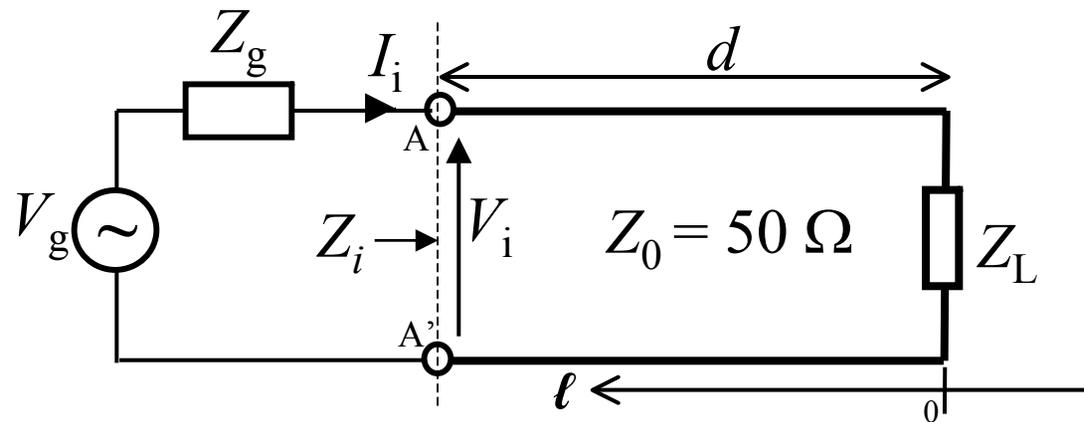
## Example 2

A lossless transmission line with  $Z_0 = 50 \Omega$  and  $d = 1.5 \text{ m}$  connects a voltage  $V_g$  source to a terminal load of  $Z_L = (50 + j50) \Omega$ . If  $V_g = 60 \text{ V}$ , operating frequency  $f = 100 \text{ MHz}$ , and  $Z_g = 50 \Omega$ , find the distance of the first voltage maximum  $\ell_M$  from the load. What is the power delivered to the load  $P_L$ ? Assume the speed of the wave along the transmission line equal to speed of light,  $c$ .



## Solutions

The following information is given:

$$Z_0 = 50\Omega, \quad d = 1.5 \text{ m},$$

$$V_g = 60 \text{ V}, \quad Z_g = 50\Omega, \quad Z_L = 50 + j50\Omega,$$

$$f = 100\text{MHz} = 10^8 \text{ Hz}$$

$$u_p = c \quad \Rightarrow \quad \lambda = \frac{c}{10^8} = 3 \text{ m}$$

The reflection coefficient at the load is:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{50 + j50 - 50}{50 + j50 + 50} = 0.2 + j0.4 = 0.45e^{j1.11}$$

Therefore,  $|\Gamma_L| = 0.45$ ,  $\theta_L = 1.11$  rad

Then, 
$$\ell_M = \frac{\theta_L \lambda}{4\pi} + \frac{n\lambda}{2}, \quad \text{when } n = 0$$
$$= \frac{1.11\lambda}{4\pi} = 0.09\lambda = 0.27 \text{ m (from the load)}$$

The input impedance  $Z_i$  looking at the input to the transmission line is:

$$Z_i = Z_0 \frac{Z_L + jZ_0 \tan(kd)}{Z_0 + jZ_L \tan(kd)}$$

$$Z_i = 50 \frac{50 + j50 + j50 \tan\left(\frac{2\pi}{3} \times 1.5\right)}{50 + j(50 + j50) \tan\left(\frac{2\pi}{3} \times 1.5\right)} = 50 + j50 \Omega$$

The current at the input to the transmission line is :

$$I_i = \frac{V_g}{Z_g + Z_i} = \frac{60}{50 + 50 + j50} = 0.48 - j0.24 \text{ A}$$

As the transmission line is lossless, power delivered to the load  $P_L$  is equal to the power input to the transmission line  $P_i$ . Hence,

$$P_L = P_i = \frac{1}{2} |I_i|^2 \operatorname{Re}\{Z_i\} = \frac{1}{2} \times 0.288 \times 50 = 7.2 \text{ W}$$

## 6.3 Complete solutions for voltage and current

The voltage and current on the transmission line can be written as:

$$V(\ell) = V_0^+ e^{jkl} + V_0^- e^{-jkl} = V_0^+ e^{jkl} (1 + \Gamma_L e^{-j2k\ell})$$

$$I(\ell) = \frac{V_0^+}{Z_0} e^{jkl} - \frac{V_0^-}{Z_0} e^{-jkl} = \frac{V_0^+}{Z_0} e^{jkl} (1 - \Gamma_L e^{-j2k\ell})$$

We still have one unknown  $V_0^+$  in  $V(\ell)$  and  $I(\ell)$ . We need the knowledge of voltage source  $V_g$  to further determine  $V_0^+$ .

At  $\ell = d$ ,  $V(d) = V_i$  and  $I(d) = I_i$ .

$$V_i = V_0^+ e^{jkd} (1 + \Gamma_L e^{-j2kd}) \quad I_i = \frac{V_0^+}{Z_0} e^{jkd} (1 - \Gamma_L e^{-j2kd})$$

$V_i$  and  $I_i$  are related to the source voltage  $V_g$  as:

$$V_g = V_i + I_i Z_g$$

From the expressions of  $V_i$ ,  $I_i$ , and  $V_g$ , we can find  $V_0^+$ .

$$V_0^+ = \frac{V_g Z_0 e^{-jkd}}{(Z_g + Z_0)(1 - \Gamma_g \Gamma_L e^{-j2kd})}$$

$$\Gamma_g = \frac{Z_g - Z_0}{Z_g + Z_0} = \text{source reflection coefficient}$$

Putting  $V_0^+$  into the expressions of  $V(\ell)$  and  $I(\ell)$ , we have:

$$V(\ell) = \frac{V_g Z_0 e^{-jkd}}{(Z_g + Z_0)(1 - \Gamma_g \Gamma_L e^{-j2kd})} e^{jkl} (1 + \Gamma_L e^{-j2kl})$$
$$I(\ell) = \frac{V_g e^{-jkd}}{(Z_g + Z_0)(1 - \Gamma_g \Gamma_L e^{-j2kd})} e^{jkl} (1 - \Gamma_L e^{-j2kl})$$


Now the voltage and current on the transmission line are expressed in terms of the known parameters of the transmission line.

### Example 3

A 1.05-GHz generator circuit with a series impedance  $Z_g = 10\Omega$  and voltage source given by:

$$v_g(t) = 10 \sin(\omega t + 30^\circ) \text{ (V)}$$

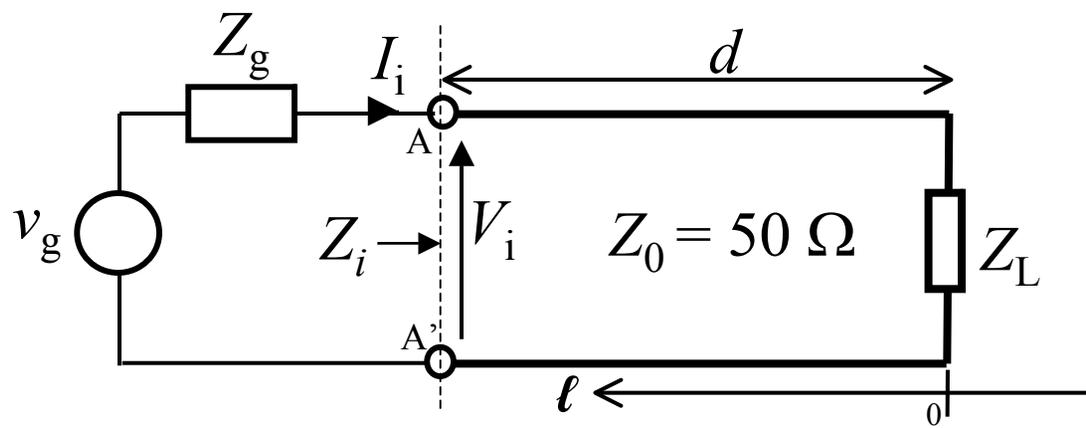is connected to a load  $Z_L = (100 + j50)$  through a 50- $\Omega$ , 67-cm-long lossless transmission line. The phase velocity of the line is  $0.7c$ , where  $c$  is the velocity of light in a vacuum. Find the instantaneous voltage and current  $v(\ell, t)$  and  $i(\ell, t)$  on the line and the average power delivered to the load.



## Solutions

$$\lambda = \frac{u_p}{f} = \frac{0.7 \times 3 \times 10^8}{1.05 \times 10^9} = 0.2 \text{ m}$$

$$d = 67 \text{ cm} = \frac{0.67}{0.2} = 3.35\lambda$$

source reflection coefficient  $\Gamma_g$

$$= \frac{Z_g - Z_0}{Z_g + Z_0} = \frac{10 - 50}{10 + 50} = -\frac{2}{3}$$

load reflection coefficient  $\Gamma_L$

$$= \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{100 + j50 - 50}{100 + j50 + 50} = 0.45e^{j0.46}$$

$$\begin{aligned}
 v_g(t) &= 10 \sin(\omega t + 30^\circ) \\
 &= 10 \cos(\omega t - 60^\circ) = \operatorname{Re}\{10e^{-j60^\circ} e^{j\omega t}\} \quad (\text{V})
 \end{aligned}$$

Phasor form:  $V_g = 10e^{-j\pi/3}$

$$\begin{aligned}
 V(\ell) &= \frac{V_g Z_0 e^{-jkd}}{(Z_g + Z_0)(1 - \Gamma_g \Gamma_L e^{-j2kd})} e^{jkl} (1 + \Gamma_L e^{-j2kl}) \\
 &= \frac{10e^{-j\pi/3} 50e^{-j\frac{2\pi}{\lambda}(3.35\lambda)}}{(10 + 50) \left[ 1 - (-2/3)(0.45e^{j0.46}) e^{-j\frac{4\pi}{\lambda}(3.35\lambda)} \right]} \times \\
 &\quad \left[ e^{jkl} + (0.45e^{j0.46}) e^{-jkl} \right] = 10.18e^{j2.77} \left[ e^{jkl} + 0.45e^{-j(k\ell - 0.46)} \right]
 \end{aligned}$$

$$\begin{aligned}
 I(\ell) &= \frac{V_g e^{-jkd}}{(Z_g + Z_0)(1 - \Gamma_g \Gamma_L e^{-j2kd})} e^{jkl} (1 - \Gamma_L e^{-j2kl}) \\
 &= 0.20 e^{j2.77} \left[ e^{jkl} - 0.45 e^{-j(kl-0.46)} \right]
 \end{aligned}$$

Therefore instantaneous forms are:

$$\begin{aligned}
 v(\ell, t) &= \text{Re}\{V(\ell)e^{j\omega t}\} \\
 &= \text{Re}\{10.18 e^{j2.77} [e^{jkl} + 0.45 e^{-j(kl-0.46)}] e^{j\omega t}\} \\
 &= 10.18 \cos(\omega t + k\ell + 2.77) + 4.58 \cos(\omega t - k\ell + 3.23)
 \end{aligned}$$

$$\begin{aligned}
 i(\ell, t) &= \text{Re}\{I(\ell)e^{j\omega t}\} \\
 &= \text{Re}\{0.20 e^{j2.77} [e^{jkl} - 0.45 e^{-j(kl-0.46)}] e^{j\omega t}\} \\
 &= 0.20 \cos(\omega t + k\ell + 2.77) - 0.09 \cos(\omega t - k\ell + 3.23)
 \end{aligned}$$

$$\begin{aligned}
 Z_i &= Z_0 \frac{Z_L + jZ_0 \tan(kd)}{Z_0 + jZ_L \tan(kd)} \\
 &= 50 \frac{(100 + j50) + j50 \tan\left(\frac{2\pi}{\lambda} \times 3.35\lambda\right)}{50 + j(100 + j50) \tan\left(\frac{2\pi}{\lambda} \times 3.35\lambda\right)} \\
 &= 21.9 + j17.4 \Omega
 \end{aligned}$$

$$I_i = \frac{V_g}{Z_g + Z_i} = \frac{10e^{-j\pi/3}}{10 + 21.9 + j17.4} = 0.28e^{-j1.55}$$

$$\begin{aligned} & \text{Power delivered to the load} \\ &= \text{power input to the transmission line at AA}' \\ &= \frac{1}{2} \operatorname{Re}\{V_i I_i^*\} \\ &= \frac{1}{2} \operatorname{Re}\{I_i Z_i I_i^*\} \\ &= \frac{1}{2} |I_i|^2 \operatorname{Re}\{Z_i\} \\ &= \frac{1}{2} 0.28^2 \operatorname{Re}\{21.9 + j17.4\} \\ &= 0.86 \text{ Watt} \end{aligned}$$

## 7 Special Cases of Terminations in a Transmission Line

### 7.1 Matched line

For a matched line,  $Z_L = Z_0$ . Then,


$$Z(\ell) = Z_0 \frac{Z_0 + jZ_0 \tan(k\ell)}{Z_0 + jZ_0 \tan(k\ell)} = Z_0$$

$$\Gamma(\ell) = \frac{Z(\ell) - Z_0}{Z(\ell) + Z_0} = 0$$

} for any length  $\ell$  of the line

Note  $\ell = -z$

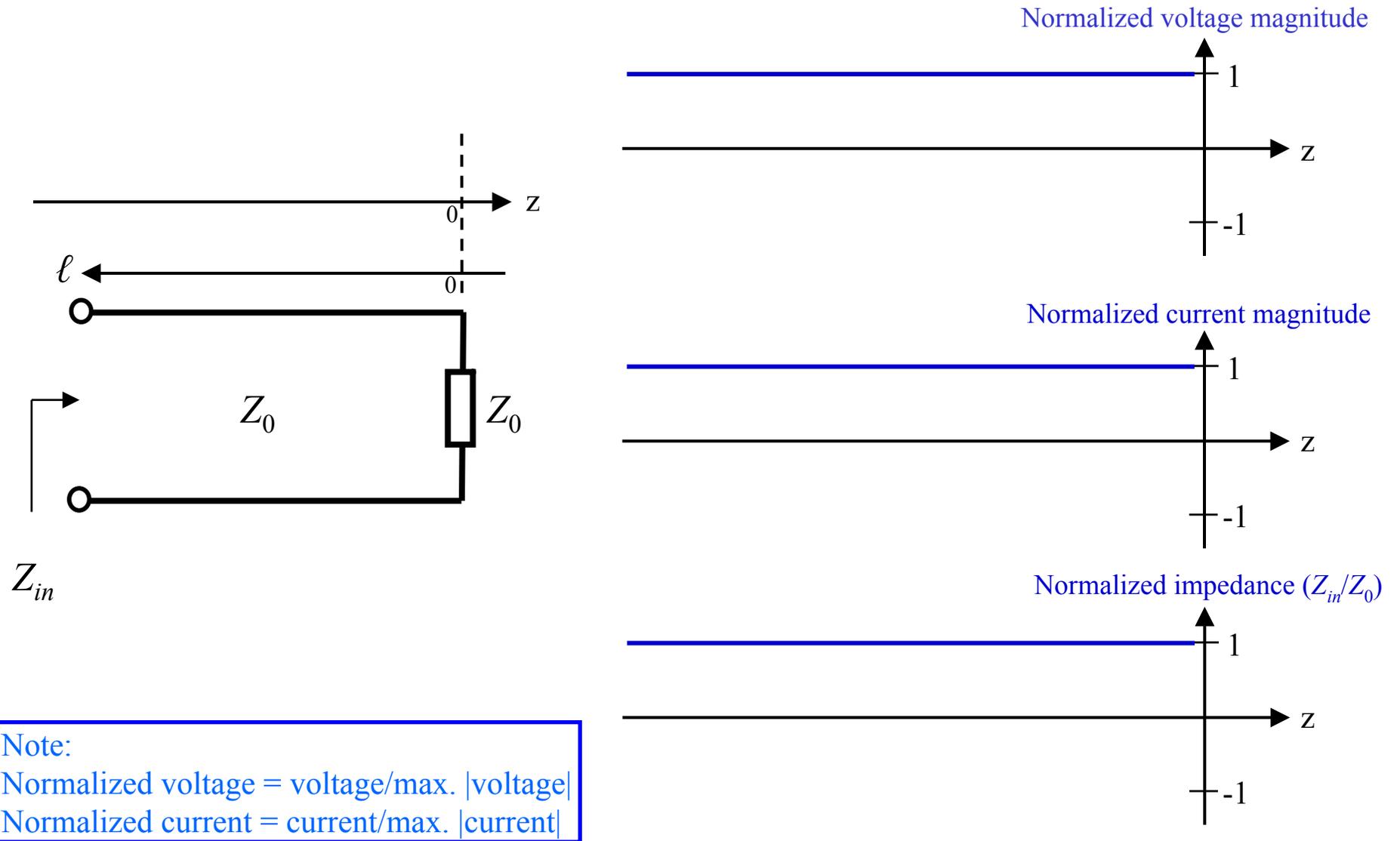
Thus, there is no reflection on a matched line. There is only an incident voltage. It is same as the case of an infinitely long line.


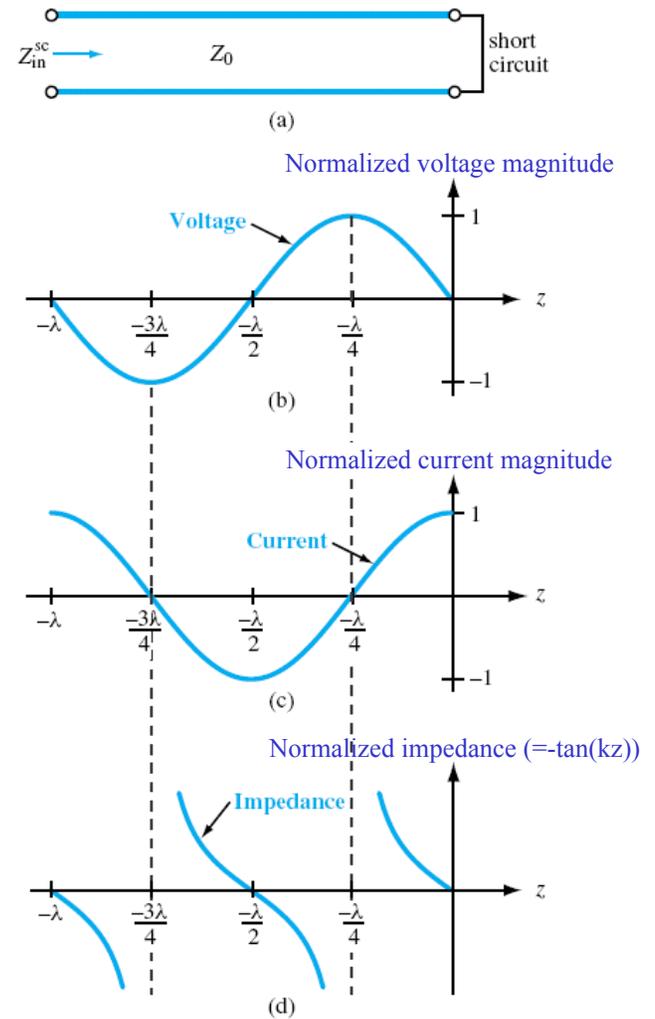
## 7.2 Short-circuited line

For a short circuit,  $Z_L = 0$ . Then

$$Z_{in}^{sc} = jZ_0 \tan(k\ell) = -jZ_0 \tan(kz)$$



## 7.3 Open-circuited line

For an open circuit,  $Z_L = \infty$ . Then


$$Z_{in}^{oc} = -jZ_0 \cot(kl) = jZ_0 \cot(kz)$$

Note that:

$$\begin{aligned} Z_{in}^{sc} Z_{in}^{oc} &= [jZ_0 \tan(kl)][-jZ_0 \cot(kl)] \\ &= Z_0^2 \end{aligned}$$


$$\begin{aligned} Z_{in}^{sc} / Z_{in}^{oc} &= [jZ_0 \tan(kl)] / [-jZ_0 \cot(kl)] \\ &= -\tan^2(kl) \end{aligned}$$

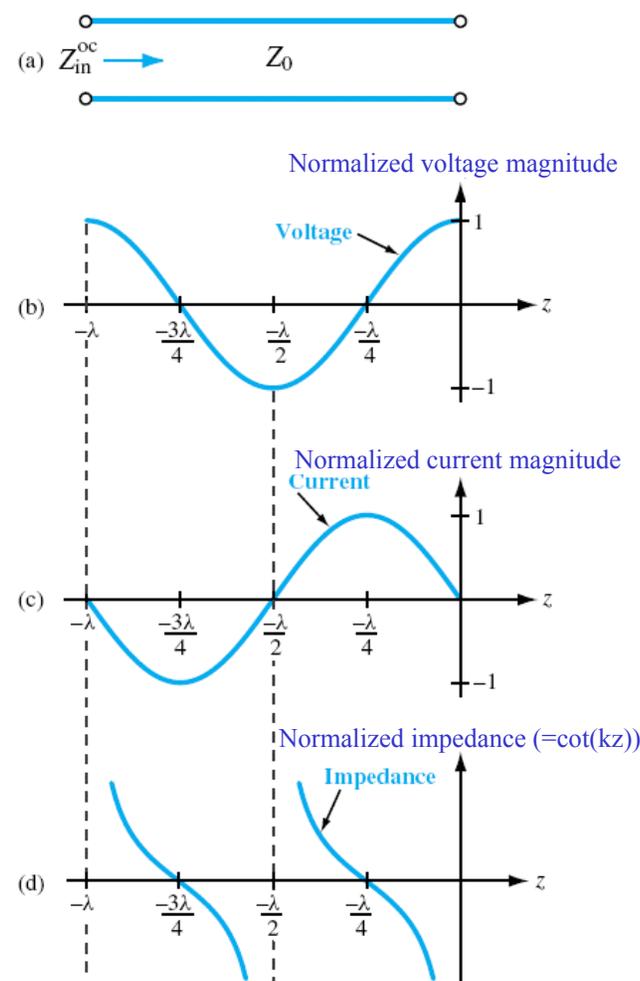Given  $Z_{in}^{sc}$ ,  $Z_{in}^{oc}$ , and  $l$ , compute  $Z_0$  and  $k$ .



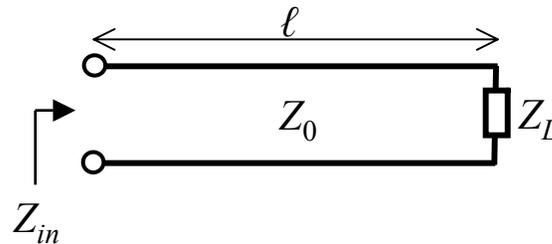
## 7.4 $\lambda/4$ transmission line terminated in $Z_L$

$$Z_{in} = Z(\ell = \lambda/4) = Z_0 \frac{Z_L + jZ_0 \tan(\pi/2)}{Z_0 + jZ_L \tan(\pi/2)} = \frac{Z_0^2}{Z_L}$$


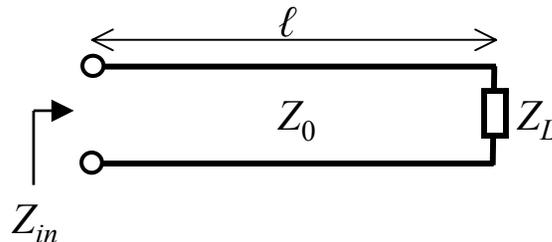
## 7.5 $\lambda/2$ transmission line terminated in $Z_L$

$$Z_{in} = Z(\ell = \lambda/2) = Z_0 \frac{Z_L + jZ_0 \tan(\pi)}{Z_0 + jZ_L \tan(\pi)} = Z_L$$



## Example 4

The open-circuit and short-circuit impedances measured at the input terminals of a lossless transmission line of length 1.5 m (which is less than a quarter wavelength) are  $-j54.6 \Omega$  and  $j103 \Omega$ , respectively.

- (a) Find  $Z_0$  and  $k$  of the line.
- (b) Without changing the operating frequency, find the input impedance of a short-circuited line that is twice the given length.
- (c) How long should the short-circuited line be in order for it to appear as an open circuit at the input terminals?

## Solution

The given quantities are

$$Z_{\text{in}}^{\text{oc}} = -j54.6 \Omega$$

$$Z_{\text{in}}^{\text{sc}} = j103 \Omega$$

$$\ell = 1.5\text{m}$$

$$(a) Z_0 = \sqrt{Z_{\text{in}}^{\text{oc}} Z_{\text{in}}^{\text{sc}}} = 75 \Omega$$

$$k = \frac{1}{\ell} \tan^{-1} \sqrt{-Z_{\text{in}}^{\text{sc}} / Z_{\text{in}}^{\text{oc}}} = 0.628 \text{ rad/m}$$

$$\lambda = \frac{2\pi}{k} = 10\text{m}$$

(b) For a line twice as long,  $\ell = 3 \text{ m}$  and  $k \ell = 1.884 \text{ rad}$ ,

$$Z_{\text{in}}^{\text{sc}} = jZ_0 \tan k\ell = -j232 \Omega$$

(c) Short circuit input impedance

$$= Z_{\text{in}}^{\text{sc}} = jZ_0 \tan(k\ell)$$

For  $Z_{\text{in}}^{\text{sc}} = \infty$ ,  $\Rightarrow k\ell = \pi/2 + n\pi$ ,  $n = 0, 1, 2, \dots$

$$\ell = \frac{\pi/2 + n\pi}{k} = \frac{2n+1}{4} \lambda$$